


# Schottky Diode Applications

**AP 4018**  
**Columbia University**

# Objectives: Schottky Diode Applications

- Schottky diodes are used in all common applications of diodes
- Additionally, Schottky diodes have higher switching speeds than PN diodes because they do not have a reverse voltage “recovery time” associated with charge storage at PN interfaces.
- For this part of the lab:

Use a Schottky Diode in a circuit

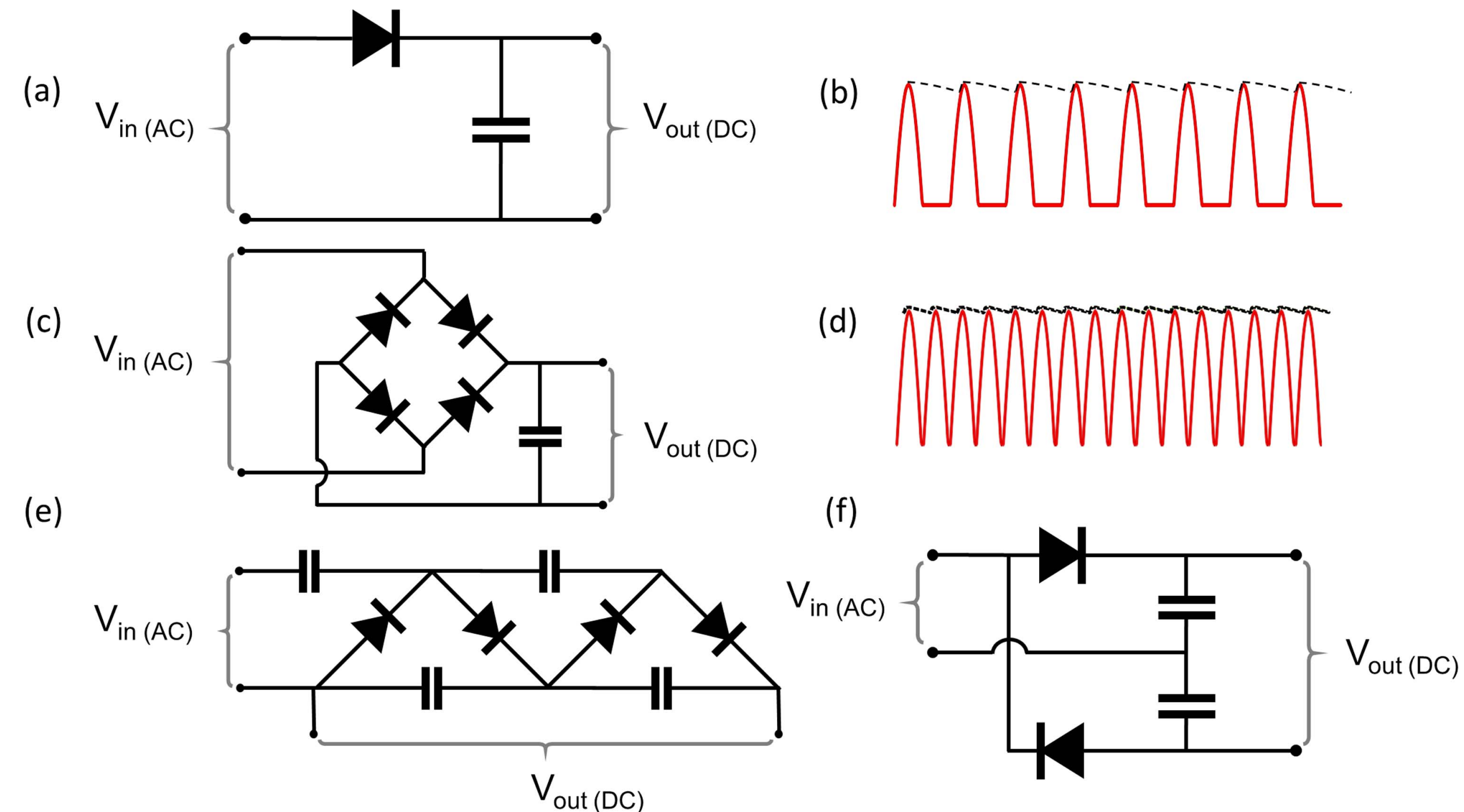

# Good reference

**OPEN ACCESS**

**IOP** Publishing

Semiconductor Science and Technology

Semicond. Sci. Technol. **32** (2017) 123002 (45pp)

<https://doi.org/10.1088/1361-6641/aa89ce>

## Topical Review

# Flexible diodes for radio frequency (RF) electronics: a materials perspective

James Semple<sup>1,5</sup>, Dimitra G Georgiadou<sup>1,5</sup> , Gwenthivir Wyatt-Moon<sup>1</sup>,  
Gerwin Gelinck<sup>2,3</sup> and Thomas D Anthopoulos<sup>1,4,5</sup> 

<sup>1</sup> Department of Physics and Centre for Plastic Electronics, Blackett Laboratory, Imperial College London, Exhibition Road, London SW7 2BW, United Kingdom

<sup>2</sup> Holst Centre/TNO, Hightech Campus 31, PO Box 8550, 5605 KN, Eindhoven, The Netherlands

<sup>3</sup> Department of Applied Physics, Eindhoven University of Technology, PO Box 513, 5600 MB, Eindhoven, The Netherlands


<sup>4</sup> Division of Physical Sciences and Engineering, King Abdullah University of Science and Technology, Thuwal 23955-6900, Saudi Arabia




# Possible Circuits

- Half-wave rectifier
- Voltage doubling (“Villard Circuit”)
- Improved voltage doubling (“Greinacher Circuit”)
- Delon voltage doubling (i.e. a diode “bridge”)
- Full-wave bridge rectifier
- Voltage quadrupler, or “charge pump”
- Also: diode logic (Or and And gates)

# Half-Wave Rectifier

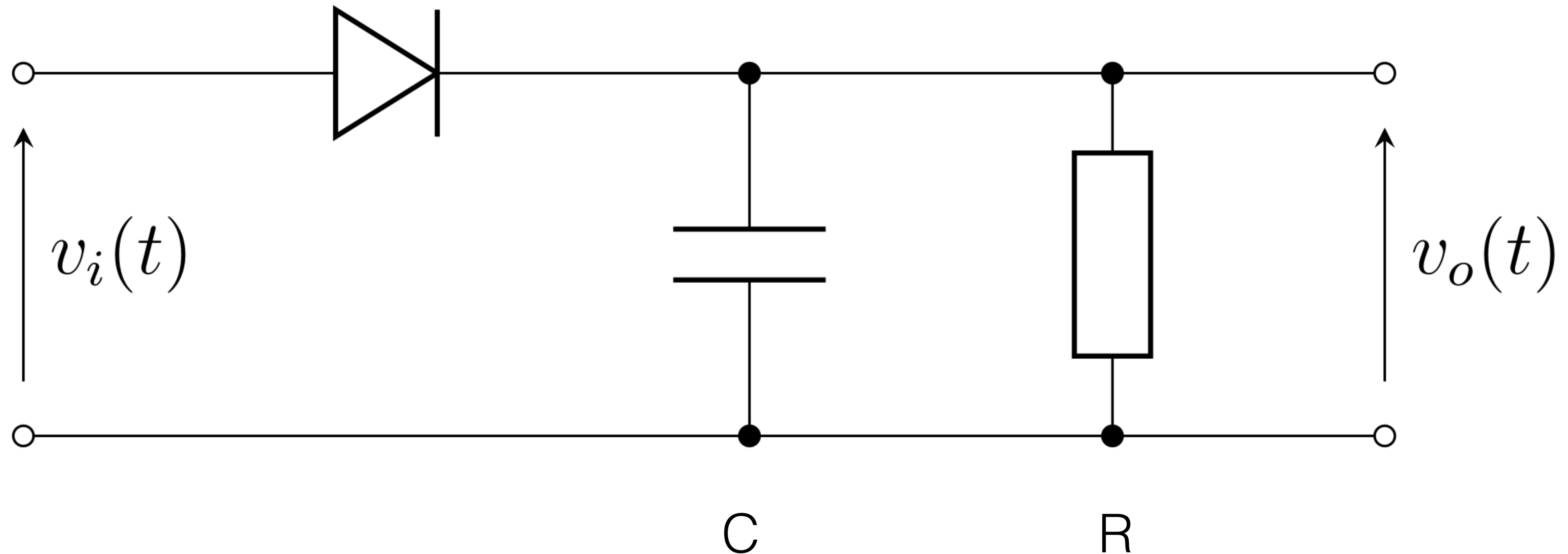


# Voltage Doubling

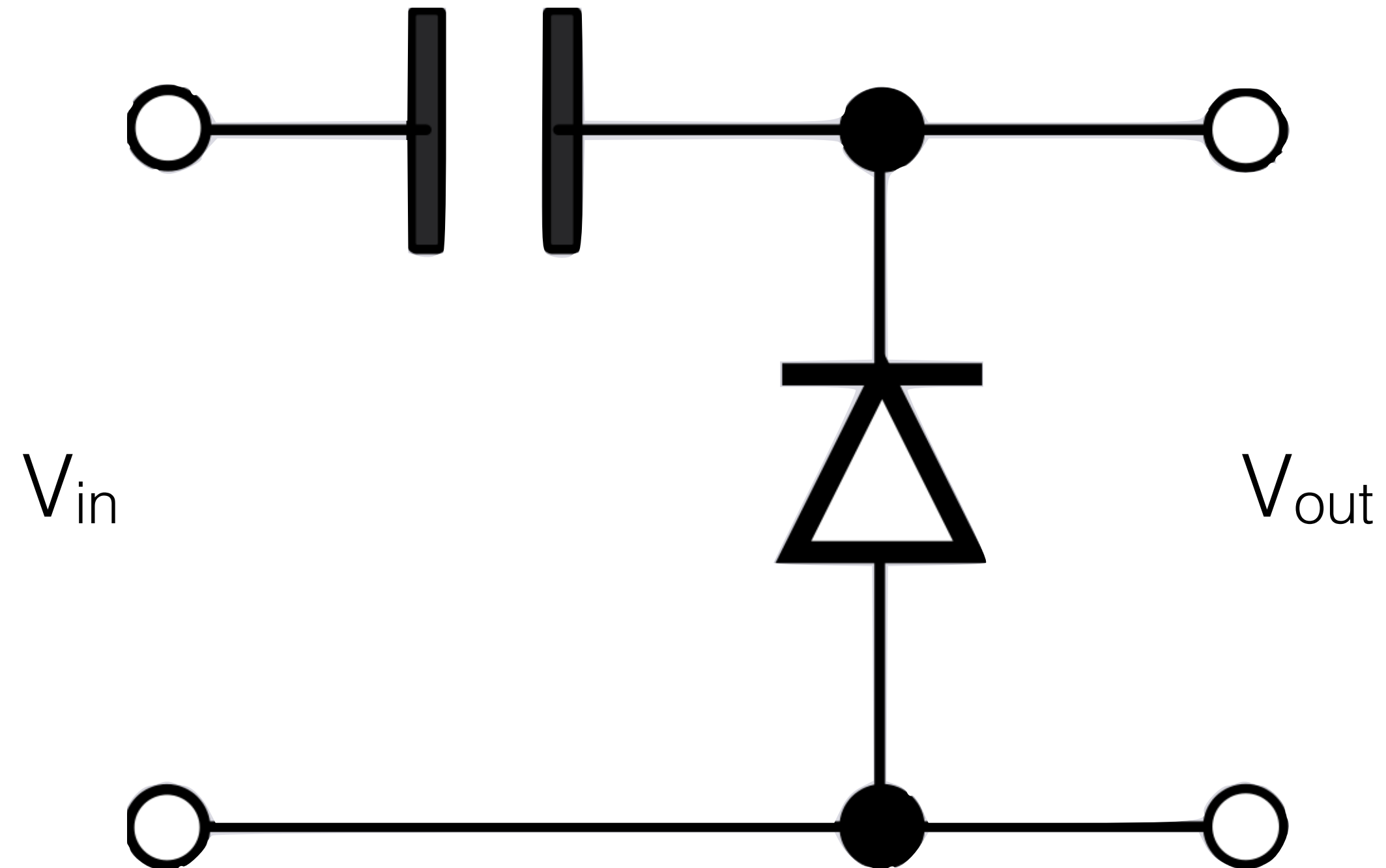




# Improved Voltage Doubling

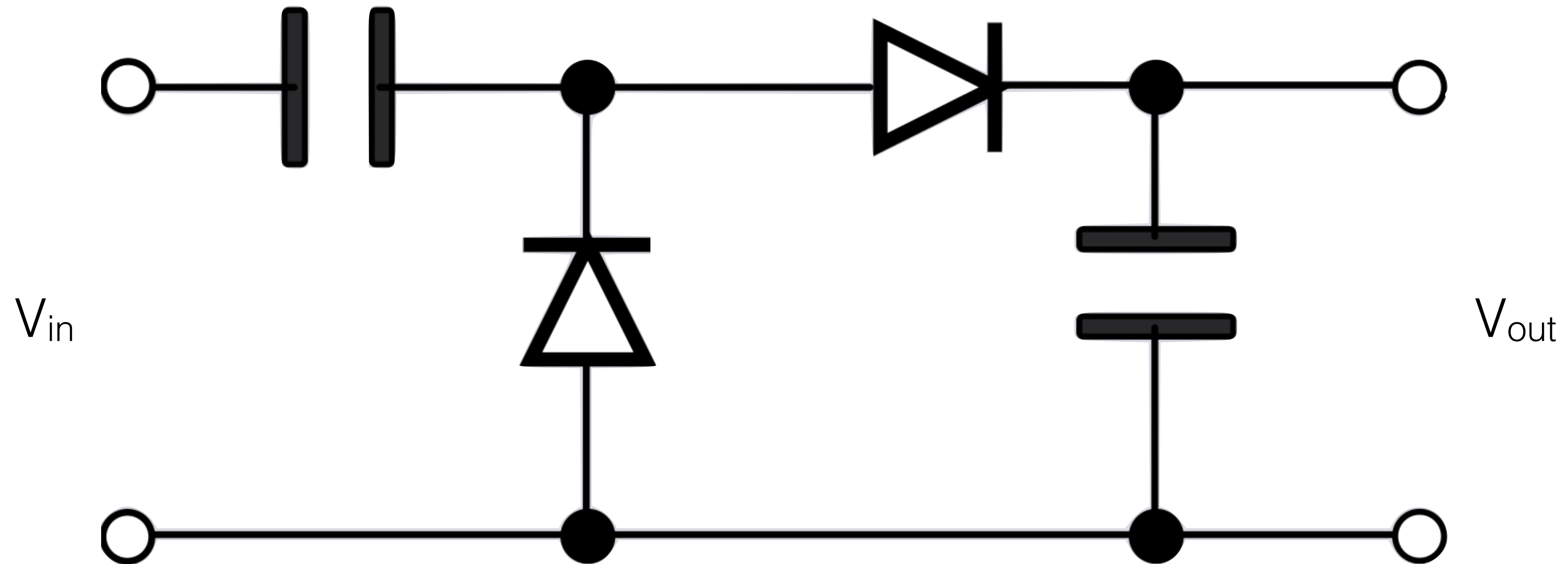



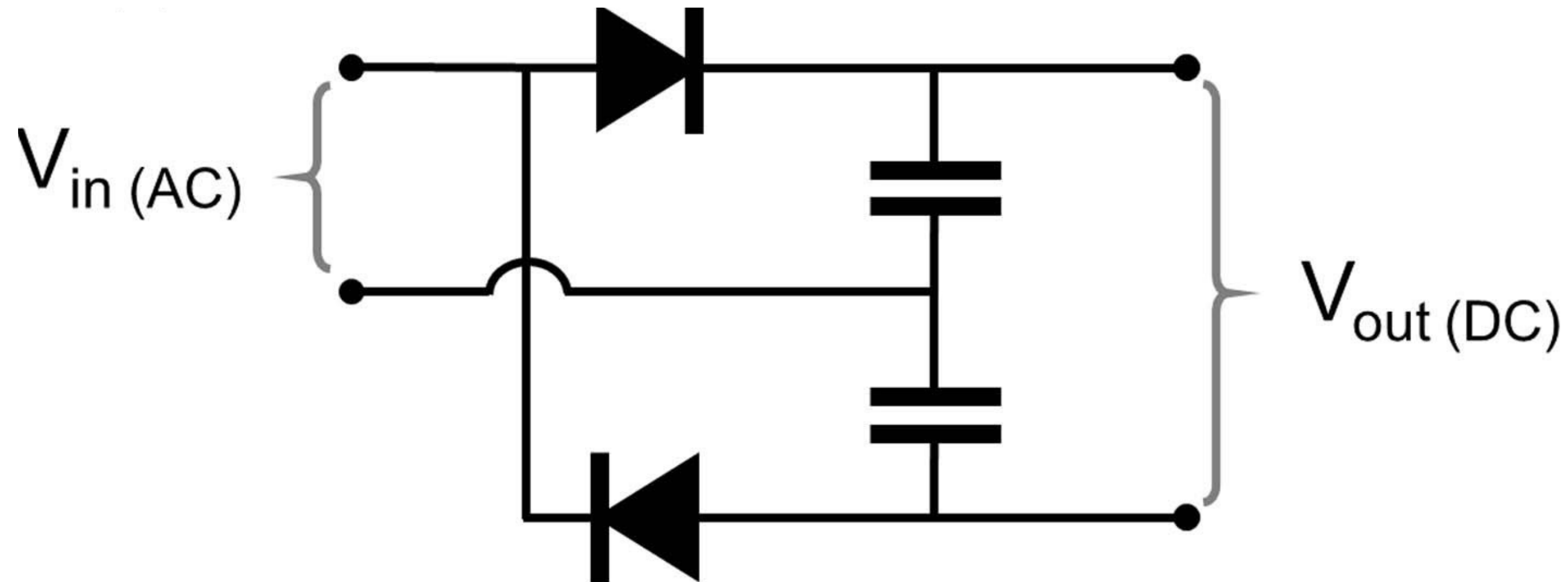
# Double Half-Wave Rectifier (Delon Voltage Doubler)






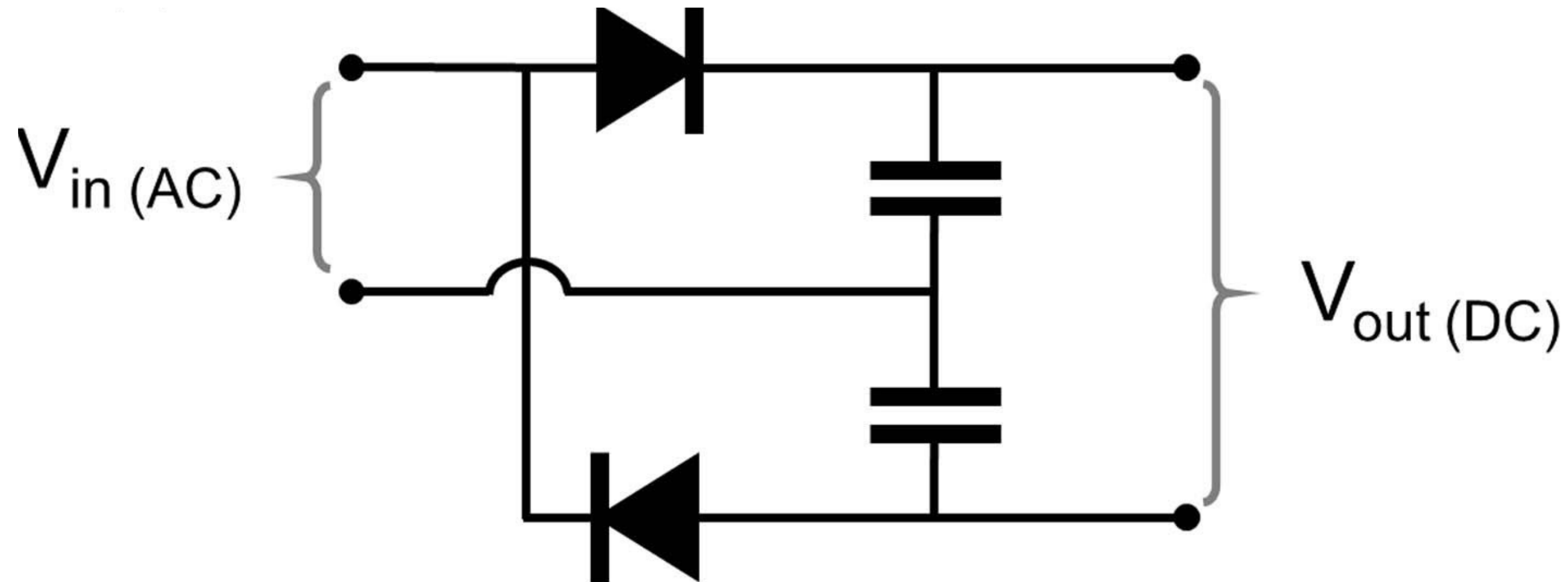
# Double Half-Wave Rectifier (Delon Voltage Doubler)



# Full-Wave Bridge Rectifier

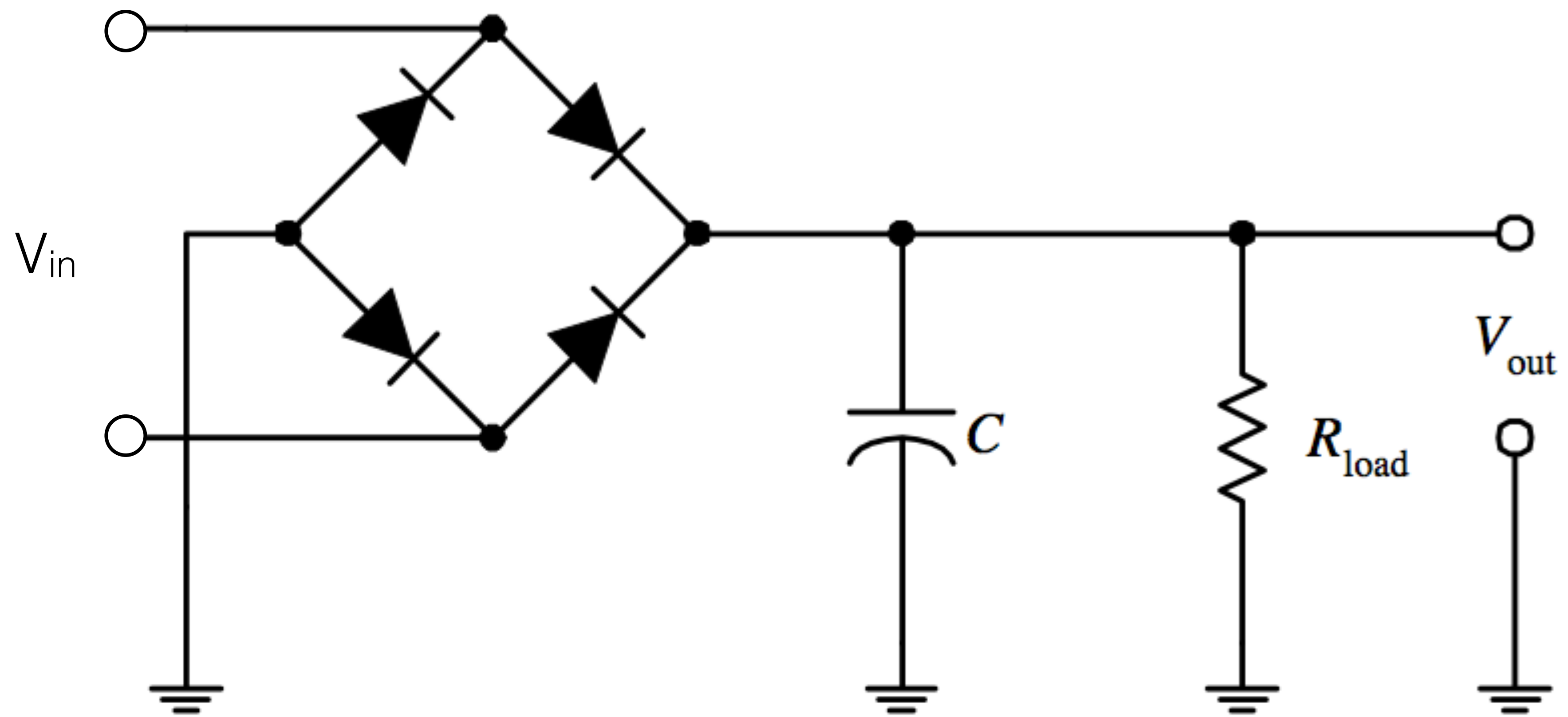

# Charge Pump

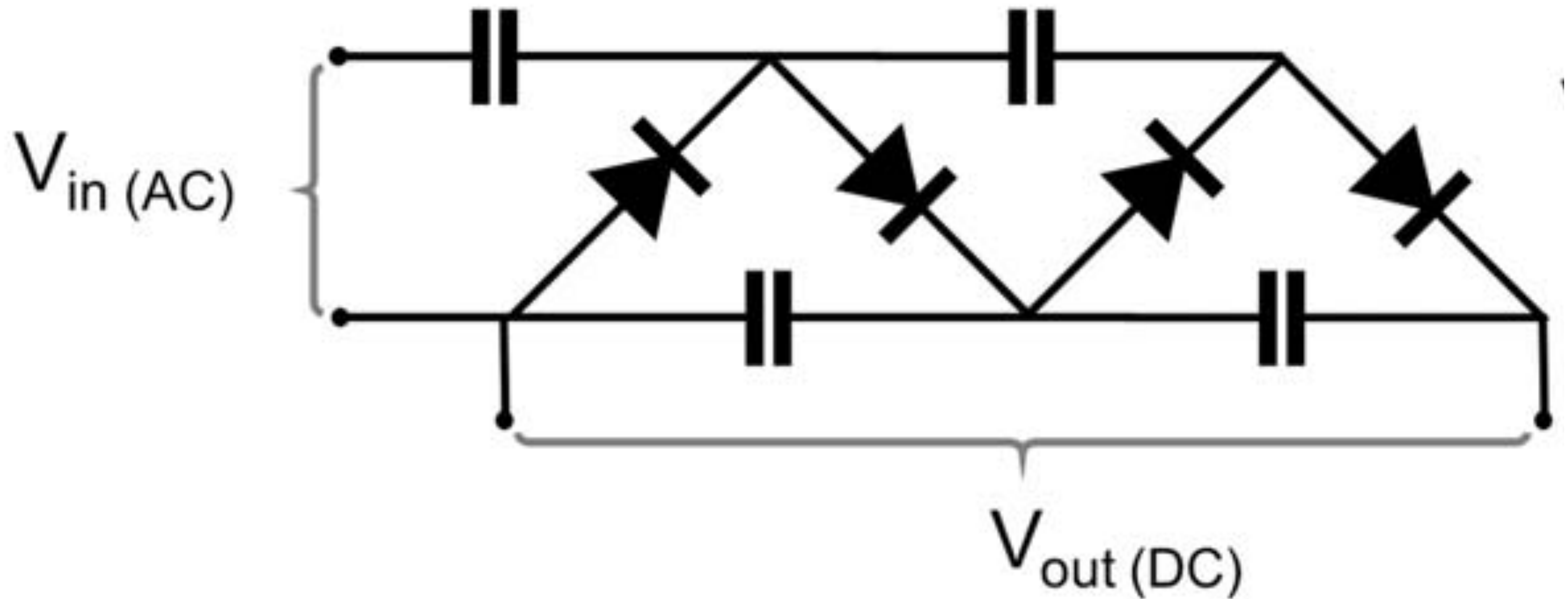



# Summary

- Make, test, and characterize one, or more, diode circuits

